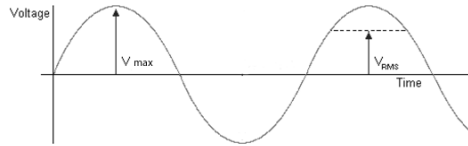


Mains Electricity

Definitions



Electricity Generation

Electricity can be generated by a coil rotating with a constant angular velocity in a uniform magnetic field – This is what happens in nearly all power stations worldwide. I_{MAX} and V_{MAX} are the maximum values of the current produced when the movement of the coils is 90° to the magnetic field. Domestic Mains electricity in New Zealand is 240 V_{rms} 50Hz (although Mains electricity actually varies between + 340 V and – 340 V). Due to energy losses at medium to high currents, electricity is converted to 330,000 Volts for transmission around NZ.


Two inductors linked by a common magnetic field are more commonly called a transformer.



Transformers can step-up or step-down Voltages with high efficiency. Effective inductors require **changing** currents so A.C. electricity is used for distribution of mains electricity for most of NZ

Equations

| | | | |
|-------------------------------------|------------------------------|-----------|----------|
| $\frac{N_p}{N_s} = \frac{V_p}{V_s}$ | Number of turns on primary | N_p | - |
| | Number of turns on secondary | N_s | - |
| $I = I_{MAX} \sin \omega t$ | Voltage across primary | V_p | V |
| | Voltage across secondary | V_s | V |
| | Current | I | A |
| | Maximum Current | I_{max} | A |
| | Angular frequency | ω | s^{-1} |
| $V = V_{MAX} \sin \omega t$ | Time | t | s |
| | Voltage | V | V |
| | Maximum Voltage | V_{max} | V |
| | Angular frequency | ω | s^{-1} |
| | Time | t | s |
| $I_{MAX} = \sqrt{2} I_{rms}$ | Maximum Current | I_{max} | A |
| | Root Mean Square Current | I_{rms} | A |
| $V_{MAX} = \sqrt{2} V_{rms}$ | Maximum Voltage | V_{max} | V |
| | Root Mean Square Voltage | V_{rms} | V |

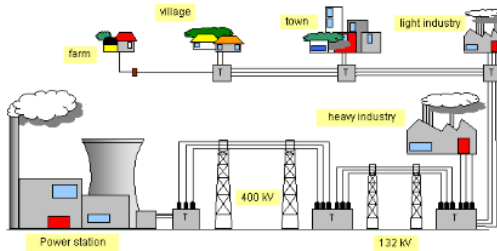

Questions


THE TRANSFORMER (2016;2)

Transformers can be used to increase or decrease the size of an AC voltage. Wei has a transformer that is designed to convert 240 V into 12.0 V.


The secondary coil has 40 turns.

- Calculate the number of turns on the primary coil.
- Explain how an alternating voltage across the primary coil creates an alternating current in a light bulb connected to the secondary coil.

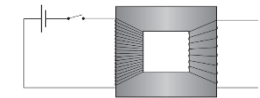Each coil of a transformer acts as an inductor. A primary coil is attached to a battery and switch as shown in the diagram below. The switch is closed and then some time later the switch is opened.



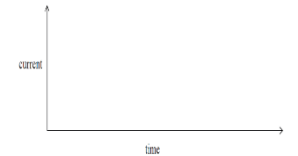
- Sketch a graph showing how the current in the coil changes when the switch is closed and then some time later is opened. Give a comprehensive explanation for the shape of your graph.



Terms

Tips

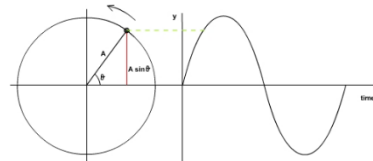- Mains A.C. electricity can be described by drawing a sine wave with time period 0.02 s – it is best drawn using phasors.



Answers

- $$\frac{N_p}{N_s} = \frac{V_p}{V_s}$$

$$N_p = \frac{V_p}{V_s} \times N_s = \frac{240}{12} \times 40 = 800 \text{ turns}$$
- An alternating voltage across the primary causes an an alternating magnetic flux in the core, which causes an alternating voltage in the secondary, which causes a current in the lamp
- When the switch closes, there is an increase in current which causes a back emf that opposes the current change. This causes the current to rise gradually. When the current reaches a maximum value, there is no flux change and no induced emf. The current is limited only by the resistance. When the switch opens, there is an open circuit; this means the current must drop to zero (almost) instantaneously.

